

## ECE2029 --- Introduction to Digital Circuit Design

### Homework 3: **Due by 12 pm Friday 22 Nov 2013**


(place completed homework in the 2029 box outside MY office AK-011)

**To ensure proper grading & return, attach the cover sheet to the FRONT of your homework**


- Always complete the reading assignments before attempting the homework problems.
- Show all of your work. Underline, circle or box each result.
- Always write neatly. The grader can not be expected to GUESS what you meant to do!
- Points are as indicated.

#### Problem 1 (10 pts)

 a) The circuit below uses a generic 3-to-8 decoder (see Vahid 2.9, class notes). What is the logic function  $F$  produced by this circuit? Complete a truth table and derive the logic expression of  $F$  (with  $S_0$ ,  $S_1$  and  $S_2$  as input and  $F$  as output). Notice that the decoder is *enabled*.



 b) What is the logic expression implemented by the circuit below?



**Problem 2 (10 pts)**

- Design an 8-to-1 by 1 bit MUX using two 4-to-1 by 1 bit multiplexers with enables. (*Hint: Use the enables, EN*).
- Design a 4-to-1 by 4 bit MUX using four 4-to-1 by 1 bit multiplexers;


**Problem 3 (10 pts)** For logic expression  $G = \bar{X} Y \bar{Z} + \bar{Y} Z + X \bar{Z}$ 

- What is the full sum of minterm expression for F?
- Use a 3-to-8 Decoder plus an OR gate to implement F.

**Problem 4 (10 pts)** = Vahid 2.76**Problem 5 (10 pts)**

Fill in the truth table for this circuit

A2	A1	A0	Z

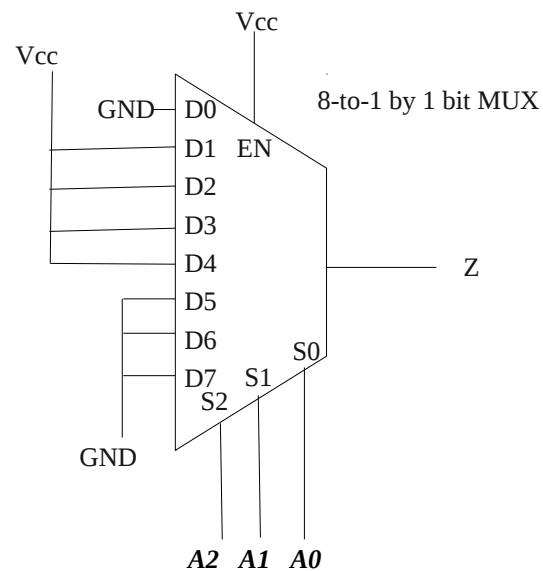**Problem 6 (10 pts)**

- Implement the logic function given by the truth table in Problem 5 in complete Verilog module using Boolean assign statements.
- Implement the logic function given by the truth table in Problem 5 in complete Verilog module using conditional statements.

**Problem 7** (10 pts)

a) Determine the shortest and worst case propagation delays for the circuit in Figure 2.17b (pg 49) assuming that  $t_{p_{and}} = 1.5 \text{ ns}$ ,  $t_{p_{or}} = 1.5 \text{ ns}$  and  $t_{p_{not}} = 1.25 \text{ ns}$ .


b) Draw a timing diagram showing the effects of the inputs  $a = 0, b = 0, c = 1$  transitioning to  $a = 1, b = 0, c = 1$  then transitioning to  $a = 1, b = 0, c = 0$ .

**Problem 8** (10 pts)

a. What logic expression  $F$  comes most directly from this logic circuit?

b. Use a Karnaugh Map to identify any potential Static Hazards in this circuit.

 c. Find a hazard free expression for  $F$  and draw that circuit.



**Problem 9** (10 pts)

Complete the timing diagram below for the original circuit in Problem 8 using the propagation delays given. Assume that the inputs  $X=Y=Z=1$  and input  $W$  transitions as shown. Assume each horizontal division is 1.0 ns. Circle any static hazards encountered.

	AND	OR	NOT
$t_{p_{HL}}$	2.0 ns	1.8 ns	2.2 ns
$t_{p_{LH}}$	2.0 ns	1.8 ns	2.4 ns

***A***

. . . . .


***B***

. . . . .

***C***

. . . . .

***D***

 

**$\overline{D}$**

. . . . .

***p1***

. . . . .

***p2***

. . . . .

***p3***

. . . . .

***F***

. . . . .

## ECE2029 Homework #3

**Submitted by:**\_\_\_\_\_

**ECE Box #:**\_\_\_\_\_

**Date:**\_\_\_\_\_

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
Total:	